
 


 



ENEE 244 Homework Set 10

(Due: Mon., Apr. 21, immediately preceding Class 23, Tues., Apr. 22, 2014)



1. Assume the gate propagation delay for each gate is 1 time unit, and draw the timing diagram for all of the gate outputs in response to the input signals (A, B, C) shown.



  2. Assume the gate propagation delay for each gate is 1 time unit, and draw the timing diagram for all of the gate outputs in response to the input signals (A and B) shown.



  3. Assume the gate propagation delay for each gate is 1 time unit, and draw the timing diagram for all of the gate outputs in response to the input signals (A and B) shown. Assume $A(t) = B(t) = 0, t < 0$.



Read all of Section 6.8 of Givone and read Sections 7.3.3–7.5.2; then work the following problems:

4. Prob. 6.22.
5. Prob. 6.23.
6. Prob. 6.27.
7. Prob. 6.28.
8. Prob. 6.30.
9. Prob. 7.7.
10. Prob. 7.12.