



Electrical and Computer Engineering Department
University of Maryland
 College Park, MD 20742-3285


Glenn L. Martin Institute of Technology ♦ A. James Clark School of Engineering

Dr. Charles B. Silio, Jr.
 Telephone 301-405-3668
 Fax 301-314-9281
 silio@umd.edu

ENEE 244 Homework Set 11

(Due: Mon., May 5, immediately preceding Class 27, Tues., May 6, 2014)

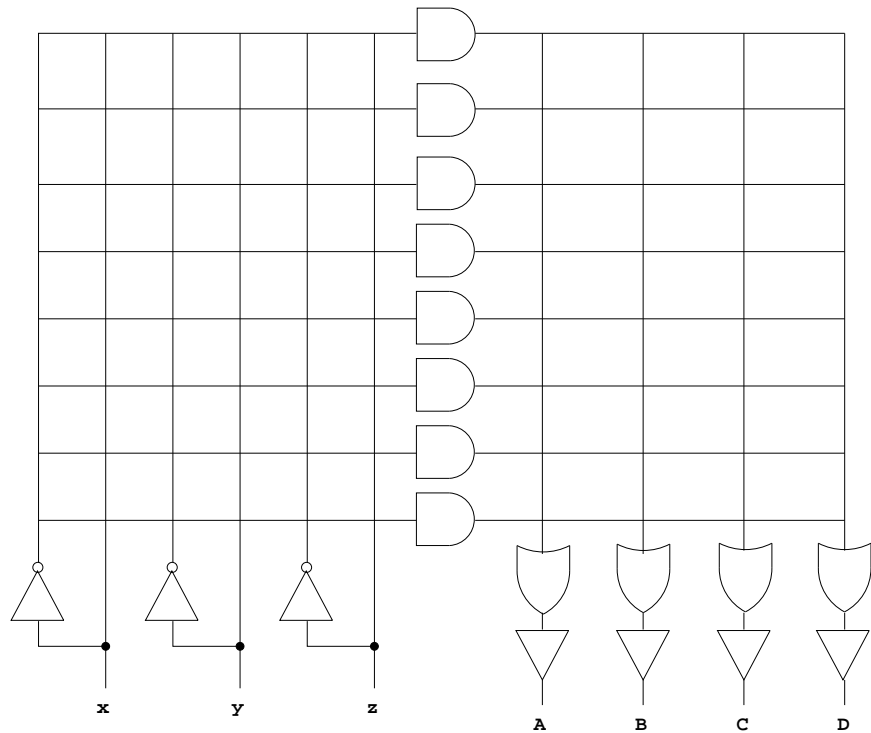1. Read Chapter 5, Sections 5-7 through 5-10 and Section 7.6.1 of Chapter 7 in Givone's text.
2. Implement the following four functions $A(x,y,z) = \Sigma(1,2,4,6)$, $B(x,y,z) = \Sigma(0,1,6,7)$, $C(x,y,z) = \Sigma(2,6)$, and $D(x,y,z) = \Sigma(1,2,3,5,7)$ by placing an X at each cross point where the fuse remains intact when implementing the four functions in the three input four output PLA shown below.



3. Work problem 5.27.
4. Work problem 5.29.
5. Work problem 5.30.
6. Work problem 5.31 a.&c.
7. Work problem 5.32.
8. Work problem 7.11.
9. Work problem 7.15.
10. Work problem 7.17.
11. Work problem 7.18.