



Electrical and Computer Engineering Department  
University of Maryland  
College Park, MD 20742-3285

Glenn L. Martin Institute of Technology  $\diamond$  A. James Clark School of Engineering

Dr. Charles B. Silio, Jr.  
Telephone 301-405-3668  
FAX 301-314-9281  
silio@umd.edu

**ENEE 244 Problem Set 7**

(Due: Mon., Mar. 31, immediately preceding Class 17, Tues., Apr. 1, 2014)

1. Design a 2-bit (binary) full adder module with 5 inputs  $a_1$ ,  $a_0$ ,  $b_1$ ,  $b_0$ , and  $c_{in}$  and with 3 outputs  $c_{out}$ ,  $s_1$ , and  $s_0$ . The module performs a binary addition of the 2-bit input  $A = a_1a_0$  with the 2-bit number  $B = b_1b_0$  and with the carry-in  $c_{in}$  to form the 2-bit sum  $S = s_1s_0$  and the carry-out  $c_{out}$ . Specify the truth table and specify the simplified output functions. (Note: this is a 5-variable Karnaugh map problem; so don't try to solve it by hooking together two 1-bit full adders.)

Tabular minimization, known also as the Quine-McCluskey method, proceeds in two steps: (1) find all prime implicants and then (2) use these prime implicants to find a minimal cost cover for the given function. Use tabular minimization to find simplest sum of products expressions for the following functions.

2.  $f(a, b, c, d) = \Sigma 0, 1, 2, 5, 9, 13, 14, 15 + \Sigma_{\phi} 8, 10, 12$

3.  $h(a, b, c, d, e, f, g) = \Sigma 20, 28, 52, 60$

4.  $h(a, b, c, d, e, f, g) = \Sigma 20, 28, 38, 39, 52, 60, 102, 103, 127$

5. Read Givone Chapt. 4, Section 4.13, excluding Section 4.13.4 covering Quine-McCluskey and tabular minimization for multiple-output functions; then work Prob. 4.33 a.

Now work the following problems from Givone, Chapt. 5:

6. Prob. 5.19.
7. Prob. 5.23.
8. Prob. 5.24.
9. Prob. 5.25.
10. Prob. 5.26.