

Homework 3

ENEE 359a: Digital VLSI Design, Spring 2007

Assigned: Fri, Mar 9; Due: Tue, Mar 13


1. Transistor Sizing

Consider a complex CMOS logic gate that implements the function $Y = \sim(ABC + DE + EFG)$.

- Draw the transistor-level schematic of the gate.
- Now optimize it: size all NMOS and PMOS transistors such that the worst-case rise and fall delays are equal to the fall delay of a minimum-sized CMOS inverter, assuming $R_p = 2.5 R_n$.

2. Logical Effort

Consider the CMOS circuit shown below.

 

- The critical path is through the inverter; ignoring the branching before this gate, use logical effort to size these gates to minimize the delay through the critical path. Assume $R_p = 2.5 R_n$ and that all FETs in series have been scaled appropriately. Assume $C_{out} = 10 C_{in}$ and that C_{in} applies to all inputs X, Y, and Z.
- What is the minimum path delay through the inverter to OUT? You can assume that $\gamma = 1$ and that the p_i terms are all equal (leave symbolically as “p” in your answer).
- How does this delay compare to the path delay from X to OUT through nand1 and nand3, now that nand3 has been optimized for the other path?